

FRANK PROGRESS AUNDEBOM
ND/ELECT/20/049

PRACTICAL MANUAL

ON

BASIC CIRCUIT DESIGN II

BY

ENGR. EBIMOBOWEI T. YABEFA


ENGR. EBIMOBOWEI T. YABEFA

BY

BASIC CIRCUIT DESIGN II


ON

PRACTICAL MANUAL

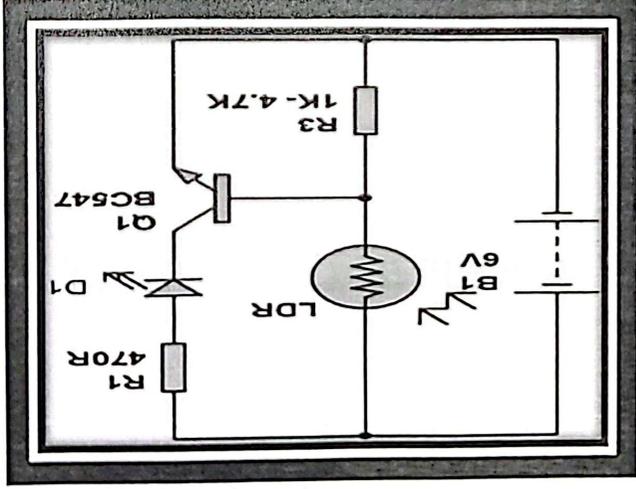


Experiment 1: Draw the breadboard and veroboard layouts of the circuit diagram shown in figure 1 below.

Experiment 2: Draw the bradboard and veroboard layouts of the circuit diagram shown in figure 2 below

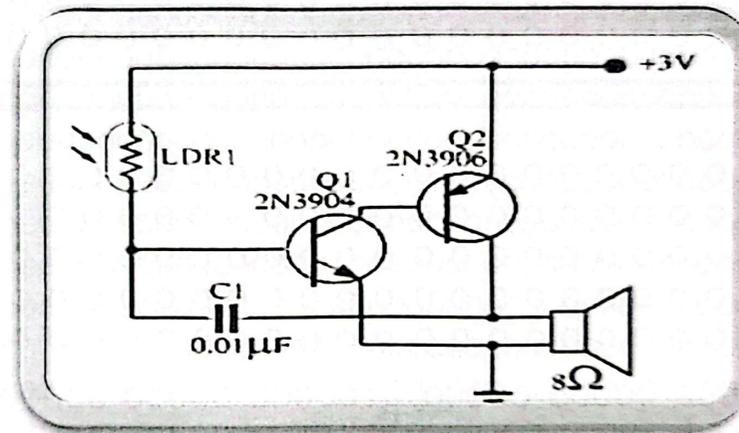

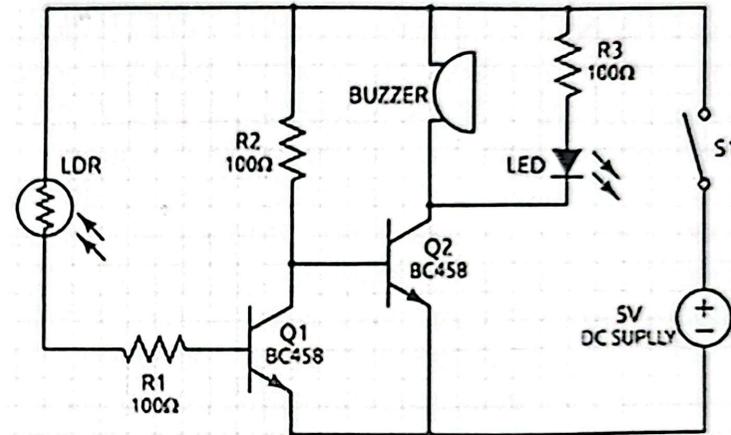Experiment 3: Draw the breadboard and veroboard layouts of the circuit diagram shown in figure 3 below.



00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
00000 00000 00000 00000 00000 00000 00000 00000 00000 00000


o
o
o
o o




o
o
o
o
o o

00000 00000 00000 00000 00000 00000 00000 00000 00000 00000
00000 00000 00000 00000 00000 00000 00000 00000 00000 00000

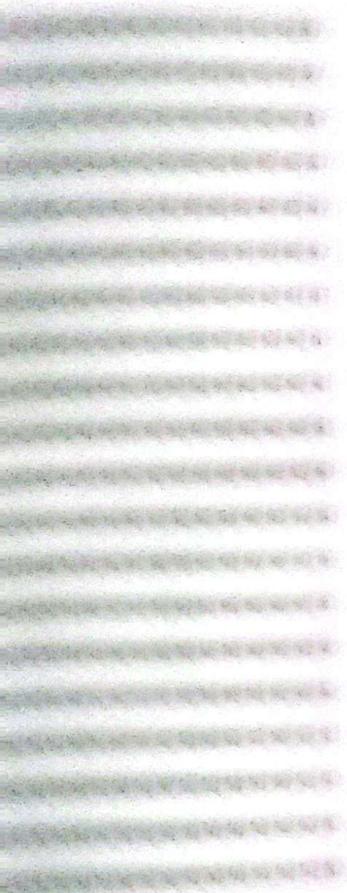
[The text in this block is extremely blurry and illegible. It appears to be a large block of text, possibly a list or a series of paragraphs, but the individual words and sentences cannot be discerned.]




Blank horizontal line

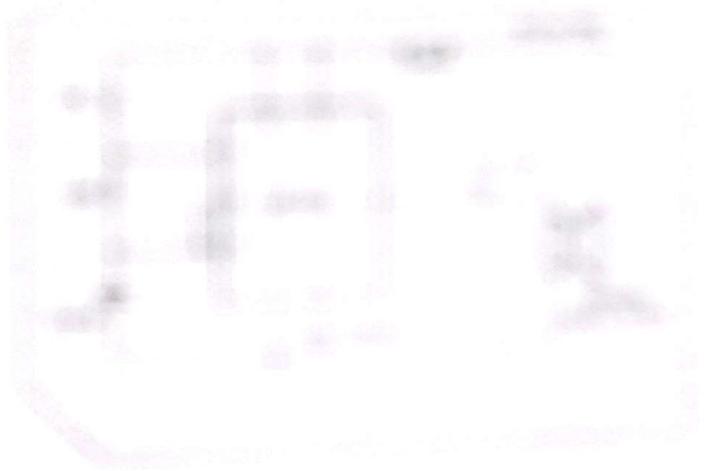

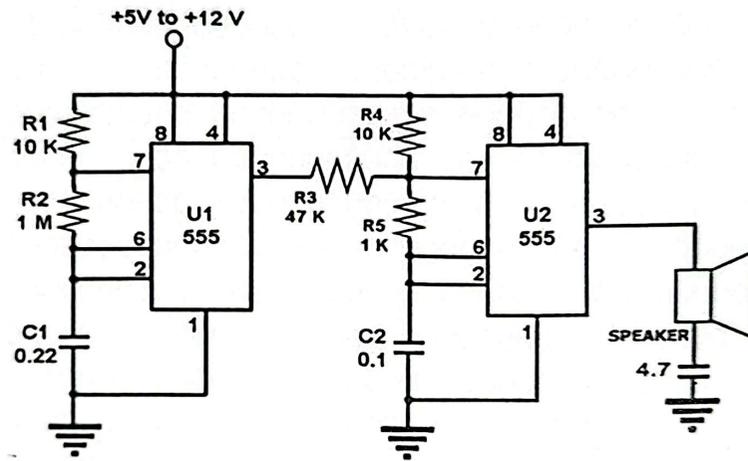Experiment 5: Draw the breadboard and veroboard layouts of the circuit diagram shown in figure 5 below.




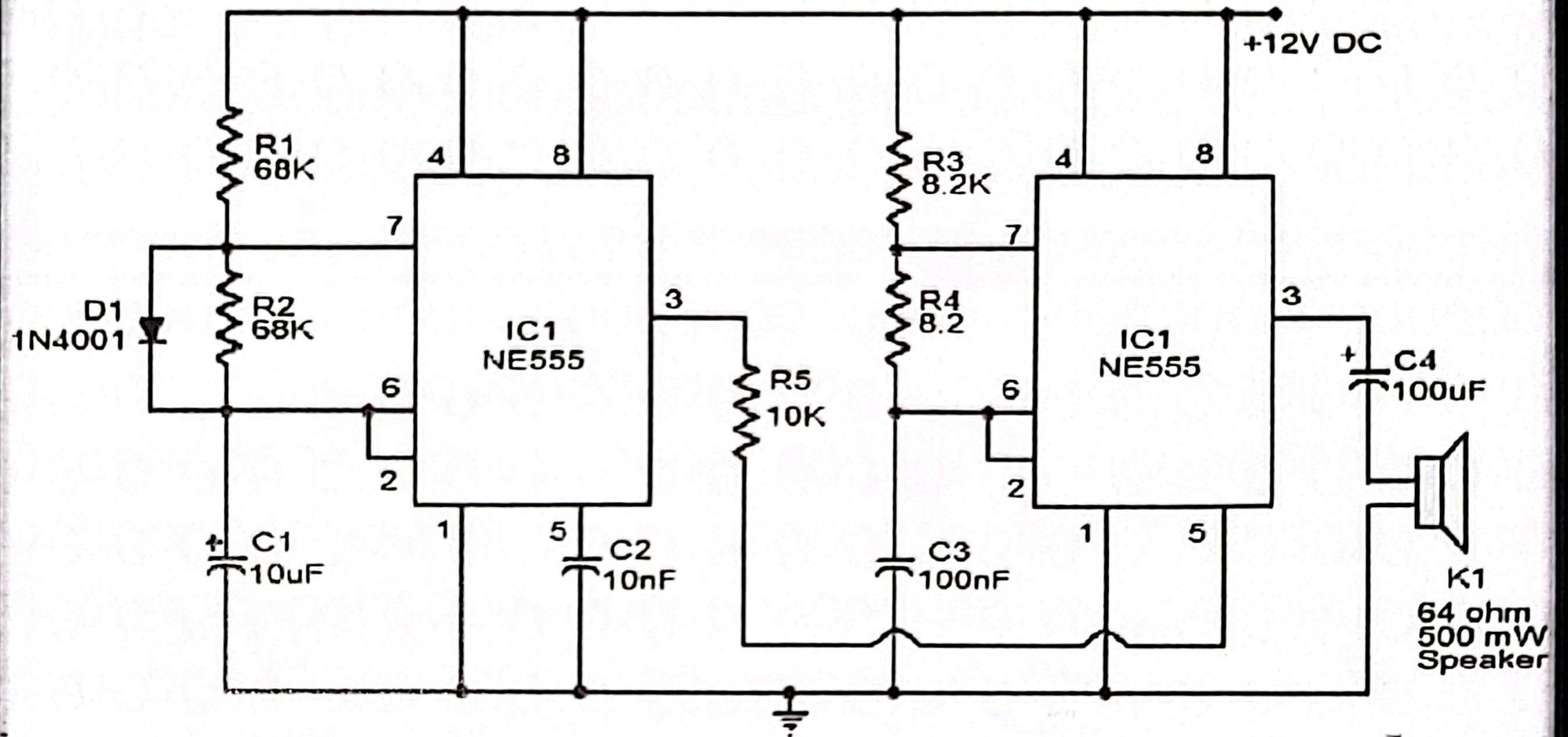


Police siren using NE555

www.circuitstoday.com

Experiment 7: Draw the bradboard and veroboard layouts of the circuit diagram shown below

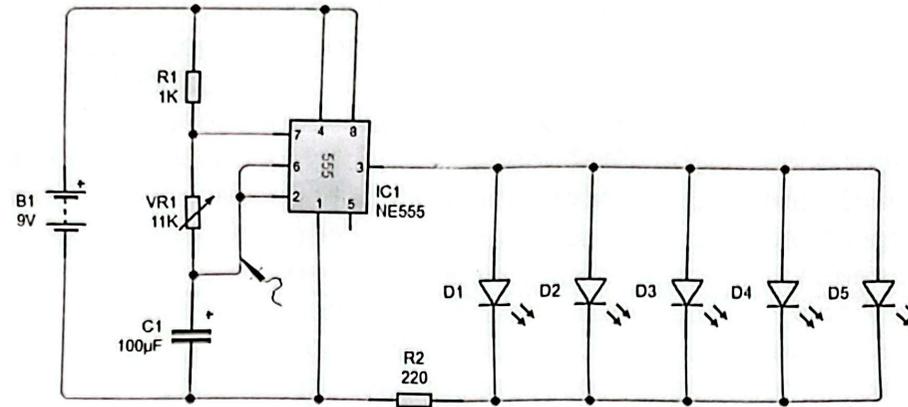

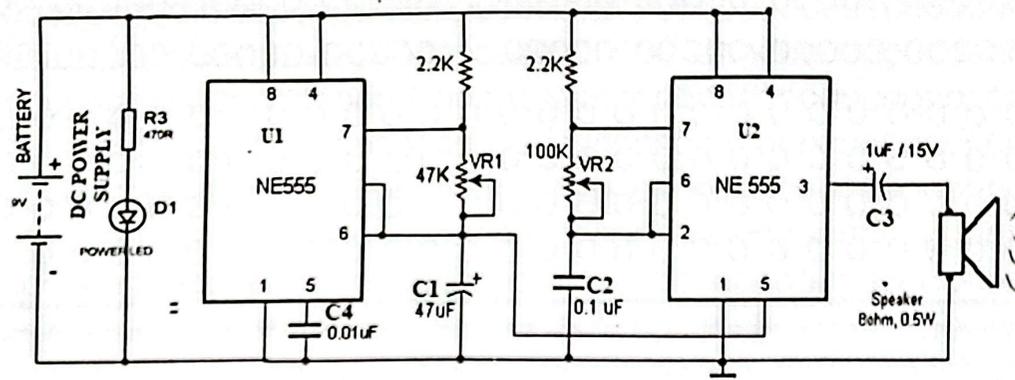Experiment 8: Draw the bradboard and veroboard layouts of the circuit diagram shown below



Precautions

For the various experiments, what were the precautions taken?

Experiment 1:

.....

.....

.....

.....

.....

Experiment 2:

.....

.....

.....

.....

.....

Experiment 3:

.....
.....
.....
.....
.....

Experiment 4:

.....
.....
.....
.....
.....

Experiment 5:

.....
.....
.....
.....
.....

Experiment 6:

.....
.....
.....
.....
.....

Experiment 7:

.....
.....
.....
.....
.....

Experiment 8:

.....
.....
.....
.....
.....

