

BAYELSA STATE POLYTECHNIC ALEIBIRI
P.M.B 168 EKEREMOR

ELECTRICAL/ELECTRONIC SYSTEMS DESIGN 1
PRACTICAL MANUAL

COURSE CODE: EEC 118

DEPARTMENT OF ELECTRICAL ELECTRONICS
ENGINEERING TECHNOLOGY.

STUDENT NAME: *BENSON AMAKIRI...@K.L.O...*

REGISTRATION NO:.....

Week 1

Aim

- i. Understanding of colour coding in resistors
- ii. Measurement of resistance.

A) Resistor colour codes not considering tolerance

| N | Band 1 | Band 2 | Band 3 | Calculated Value | Measured Value | Compare Calculated and Measured Values |
|---|----------------------------|----------------------------|--------|--|----------------|--|
| | Red | Red | Red | 2.2k Ω 560Ω | 2.182 | The calculated value is less than the measured value |
| | Yellow GREEN | Blue | Orange | 56k Ω 560Ω | 549. | |
| | White | Orange Brown | Brown | 930 Ω 910Ω | 0.897 | The calculated value is higher than the measured value |
| | Green Blue | Yellow Grey | Black | 56 Ω 68Ω | 0.67-1 | The calculated value is higher than the measured value |
| | Brown | Black | Orange | 10k Ω | 10-10 | The calculated value |

3) Using the values of the resistors given, complete the table below:

| N | Calculated Value | Colours | | | Measured Value | Tolerance Colour Value |
|---|---|---------|--------|----------------------------|----------------|------------------------|
| | | Band 1 | Band 2 | Band 3 | | |
| | 10k Ω | Brown | Black | Orange | 10-10 | |
| | 1k Ω | Brown | Black | Red | 01-00 | |
| | 68kΩ 68 Ω | Blue | Grey | Orange Black | 0.067 | |
| | 3.3k Ω | Orange | Orange | Orange | 3-278 | |
| | 100k Ω | Brown | Black | Yellow | | |

Week 2

SERIES CIRCUIT CONNECTION

Objective: Verification of series circuit current and voltages.

Procedure:

1 Connect a number of resistors of different values in series to a 5V voltage source. State the resistor values here:

2 Connect a millimeter just after the voltage source, and just before the first resistor in the series network. What is the magnitude of the current?

3 Position the millimeter between two resistors in the series network. Again, document the magnitude of the current.

What do you notice about the series current?

Series Resistance

To verify the total resistance of series connected resistors.

Take three (3) individual resistors, and measure their resistances

1) R_1 Ω

2) R_2 Ω

3) R_3 Ω

4. Form a series network with the three (3) resistors, measure the resistance of the series connected resistors by connecting one of the probes of the ohmmeter to Terminal A of the first resistors in the network, and the other probe of the ohmmeter to the terminal B of the last resistor in the series network. Record the resistance value in ohm.....

.....
.....

Sum the values of R_1 , R_2 and R_3 in ohms.....

Compare the sum of R_1 , R_2 and R_3 in (c) above, and the series resistance in b) above. Comment in the comparison.....


.....
.....

Work 3

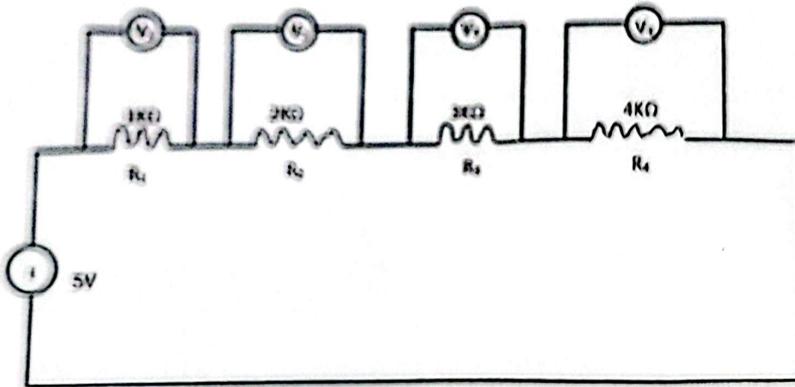QUESTION

Ohm's law is the most important mathematical relationship between voltage, current and resistance in a resistive circuit. Particularly for resistors, the law states that the voltage across a resistor is directly proportional to the current flowing through the resistor. i.e.

a series circuit consisting of four (4) resistors as shown in the circuit



Calculate the total series resistance using $R_t = R_1 + R_2 + R_3 + R_4 = 1 + 2 + 3 + 4 = 10 \text{ k}\Omega$

Calculate the series current from $I = V/R_t = \frac{10}{6} = 0.5 \text{ V}$ ✓

What are the values of the voltage drops; as indicated in the voltmeters?

-V
-V
-V
-V

d. Calculate the voltages from $V_n = IR_n$ i.e

$$V_1 = IR_1 \dots 0.5 \times 1 \dots 0.5V$$

$$V_2 = IR_2 \dots 0.5 \times 2 \dots 1V$$

$$V_3 = IR_3 \dots 0.5 \times 3 \dots 1.5V$$

$$V_4 = IR_4 \dots 0.5 \times 4 \dots 2V$$

e. What is your comment on the voltage drops, with respect to the values of the resistors in the series circuit?.....

.....

.....

.....

.....

.....

.....

.....

~~Pran~~
4/3/2021

Week 4

PARALLEL CIRCUIT CONNECTION

The main difference between a series circuit and a parallel circuit is in the way the components are connected. In a parallel circuit, there are at least two loads (resistors in this case) connected separately to the voltage source, so that the voltage across the loads are the same. But the currents in the different loads (resistors) are not the same for the parallel circuit.

The resistance of the parallel network is obtained as;

$$= \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \dots \dots \dots (1)$$


For only two resistors in parallel, the total parallel resistance is;

$$= \frac{R_1 R_2}{R_1 + R_2} \dots \dots \dots (2)$$

For three resistors in parallel, the total parallel resistance is;

$$= \frac{R_1 R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \dots \dots \dots (3)$$

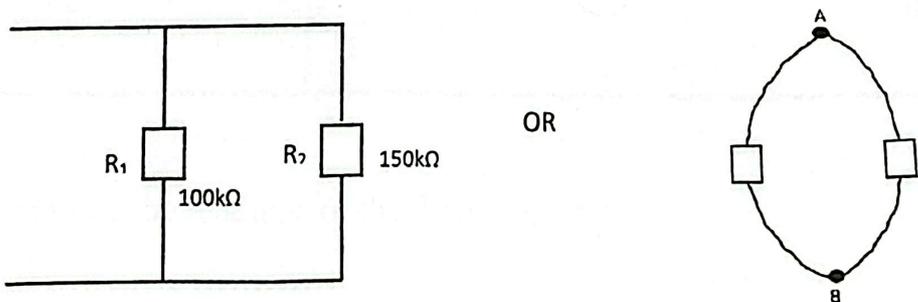Connect two resistors in parallel as shown below;



Measure the parallel resistance between test points A and B

$$R_T = \dots \dots \dots \Omega$$

Compute the parallel resistance from


$$R_T = \frac{R_1 R_2}{R_1 + R_2} = \dots\dots\dots$$

d. Comment on the total parallel resistance with respect to the resistance values of the individual resistor.....

Currents in A Parallel Circuit

Although the voltage in a parallel circuit is the same, the currents in the branches are not the same in most cases.

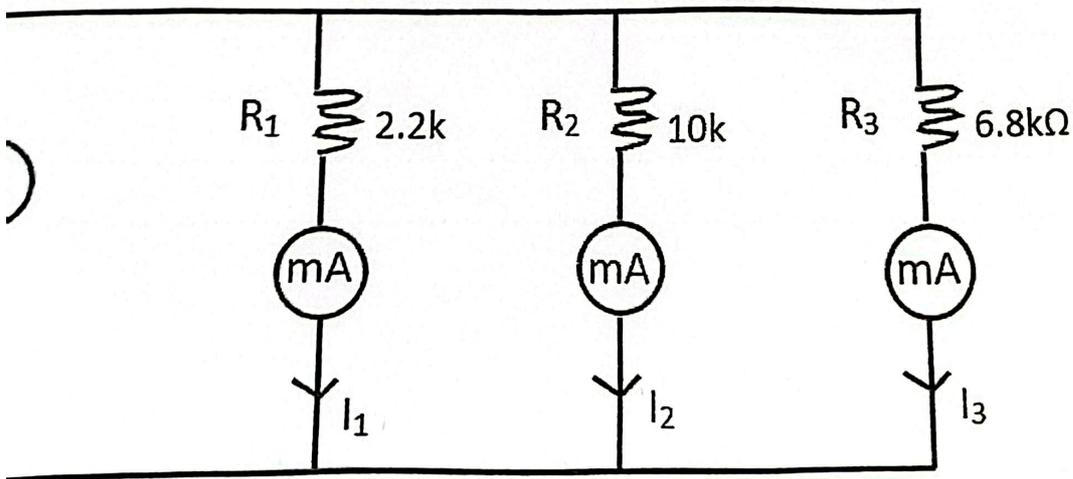Connect a parallel network of the resistors as shown below:



Compute the readings of the three milliammeters

=.....mA

=.....mA

=.....mA

c. Estimate the branch currents from the following expressions

$$I_1 = \frac{V}{R_1} = \dots\dots\dots$$

$$I_2 = \frac{V}{R_2} = \dots\dots\dots$$

$$I_3 = \frac{V}{R_3} = \dots\dots\dots$$

d. What is your comment on currents in a parallel circuit.....

.....
.....
.....
.....

e. Does your millimeter readings and the calculated values of current tally?

.....
.....

If the answer is No. why?

.....
.....

APPLICATION OF SERIES AND PARALLEL CIRCUITS


Voltage division - series

Current limitations.

Image Division

In this practical, we will see how the supply voltage of 5V is divided among the resistors connected in series. In the circuit, R_1 is a fixed valued resistor but R_2 is a variable resistor. Gradually increasing the resistance value of the variable resistor (from 0Ω to 500Ω), by turning the shaft in the clockwise direction, ensures that the circuit voltage is divided among R_1 and R_2 .

Image Division Principle

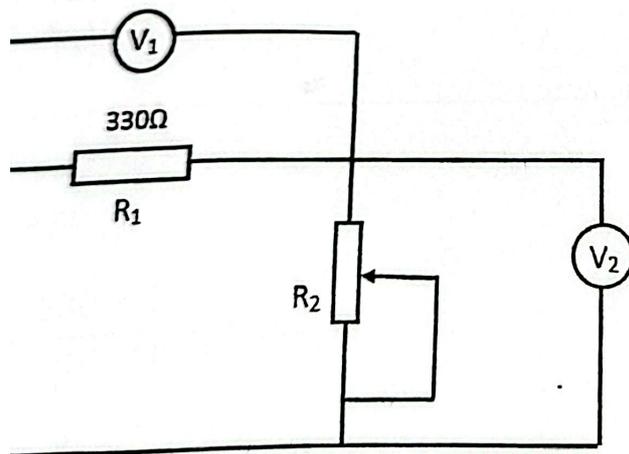

2

2

connect the circuit as shown above

- Adjust the supply voltage to 5V by turning the variable power supply
- Turn R_2 counter clockwise to the end, so that the value of RAC is zero
N/B: RAC is the resistance between the left and the center terminals of the variable resistor.
- Read the value of V_1 across R_1 and write it down in the table below.
- Turn R_2 clockwise so that RAC have different values as shown in the table below.
 Record the values of V_1 and V_2 against the value of RAC.

| Ω | 0 | 50 | 100 | 150 | 200 | 250 | 300 | 350 | 400 | 450 | 500 |
|------------|-------|-------|-------|-------|-------|-------|-----|-------|-------|-------|-------|
| Measure | | | | | | | | | | | |
| Calculated | 4.342 | 3.837 | 3.438 | 3.11 | 2.845 | 2.619 | 2.5 | 2.426 | 2.260 | 2.115 | 1.988 |
| Measure | | | | | | | | | | | |
| Calculated | 0.658 | 1.163 | 1.563 | 1.888 | 2.155 | 2.38 | 2.5 | 2.524 | 2.739 | 2.885 | 3.012 |

$$R_{AC} = 50$$

$$V_1 = \frac{330 \times 5}{330 + 50} = 4.342$$

$$V_2 = \frac{50 \times 5}{330 + 50} = 0.658$$

$$R_{AC} = 100$$

$$V_1 = \frac{(330 \times 5)}{(330 + 100)} = 3.837$$

$$V_2 = \frac{(100 \times 5)}{(330 \times 100)} = 1.163$$

$$R_{AC} = 150$$

$$V_1 = \frac{(330 \times 5)}{(330 \times 150)} = 3.438$$

$$V_2 = \frac{(150 \times 5)}{(330 \times 150)} = 1.563$$

$$R_{AC} = 200$$

$$V_1 = \frac{(330 \times 5)}{(330 \times 200)} = 3.11$$

$$V_2 = \frac{(200 \times 5)}{(330 \times 200)} = 1.888$$

$$R_{AC} = 250$$

$$V_1 = \frac{(330 \times 5)}{(330 \times 250)} = 2.845$$

$$V_2 = \frac{(250 \times 5)}{(330 \times 250)} = 2.155$$

$$R_{AC} = 300$$

$$= \frac{(330 \times 5)}{(330 \times 300)} = 2.619$$

$$= \frac{(300 \times 5)}{(330 \times 300)} = 2.38$$

3.30

$$V_1 = \frac{(330 \times 5)}{(330 \times 330)} = 2.5$$

$$V_2 = \frac{(330 \times 5)}{(330 \times 330)} = 2.5$$

$$R_{AC} = 350$$

$$V_1 = \frac{(330 \times 5)}{(330 \times 350)} = 2.426$$

$$V_2 = \frac{(350 \times 5)}{(330 \times 350)} = 2.524$$

$$R_{AC} = 400$$

$$V_1 = \frac{(330 \times 5)}{(330 \times 400)} = 2.260$$

$$V_2 = \frac{(400 \times 5)}{(330 \times 400)} = 2.739$$

$$R_{AC} = 450$$

$$V_1 = \frac{(330 \times 5)}{(330 \times 450)} = 2.115$$

$$V_2 = \frac{(450 \times 5)}{(330 \times 450)} = 2.885$$


$$R_{AC} = 500$$

$$V_1 = \frac{(330 \times 5)}{(330 \times 500)} = 1.999$$

$$V_2 = \frac{(500 \times 5)}{(330 \times 500)} = 2.972$$

Week 6

CURRENT DIVISION PRINCIPLE

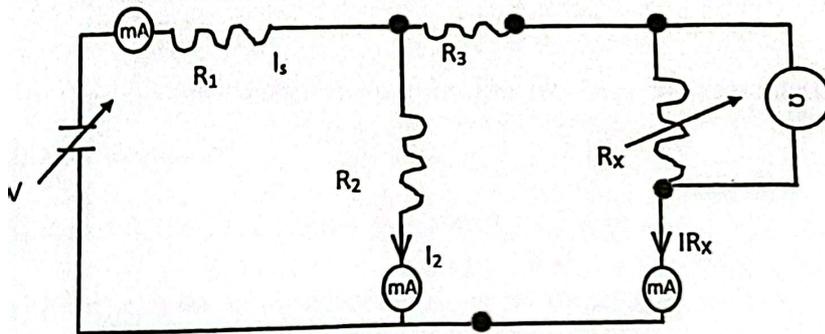

Apparatus

1. $R_1 = 1k\Omega$
2. $R_2 = 2k\Omega$
3. $R_3 = 1k\Omega$
4. $R_x = 2k\Omega$ (POT)
5. A variable power supply
6. Ohmmeter
7. Millimeter - 3ps

maximum circuit current will occur when the variable resistor is zero to zero

$$I_{1\max} = \frac{V}{R_1 + [R_2 \parallel (R_3 + R_x)]}$$

$$I_{1\max} = \frac{V}{R_1 + [R_2 \parallel R_3]} = \frac{V}{R_1 + \left(\frac{R_2 R_3}{R_2 + R_3} \right)} = \frac{9}{1 + \left[\frac{2 \times 1}{2 + 1} \right]} = \frac{9}{1.666} \text{ mA}$$

$$= 5.4 \text{ mA}$$

As maximum current of 5.4mA is expected to be shared by the branches containing the R_x (200 Ω) and the R_2 branch consisting of R_1 and R_3 in series ($R_1 + R_3$). When R_x is maximum, current in the R_2 branch will be:

$$I_2 = \frac{R_1 + R_3}{R_1 + R_2 + R_3} \times 5.4 \text{ mA} = \frac{2 + 5.4}{2 + 1 + 2} \text{ mA} = \frac{10.8}{5} = 2.16 \text{ mA}$$

By the current division principle, the R_2 branch. The maximum current in the R_2 branch would be

$$I_{2(\max)} = 5.4 \text{ mA} - 2.16 \text{ mA} = 3.24 \text{ mA}$$

(min) can be obtained when R_x is set to zero (0)

$$I_2(\min) = \frac{R_3 \times 5.4}{R_2 + R_3} \text{ mA} = \frac{1 \times 5.4}{1 + 2} = \frac{5.4}{3} \text{ mA} = 1.8 \text{ mA}$$

Complete the table below as the value of R_x is varied.

| | 0 | 100 | 150 | 200 | 400 | 600 | 800 | 1000 | 1200 | 1400 | 1600 | 1800 | 2000 |
|------------|---|------|-----|------|------|------|------|------|------|------|------|------|------|
| Measure | | | | | | | | | | | | | |
| Calculated | | 5.26 | | 5.14 | 4.93 | 4.76 | 4.62 | 4.5 | 4.39 | 4.30 | 4.22 | 4.16 | 4.09 |
| Measure | | | | | | | | | | | | | |
| Calculated | | | | | | | | | | | | | |
| Measure | | | | | | | | | | | | | |
| Calculated | | | | | | | | | | | | | |

R_X can be obtained from the expression

$$R_X = \frac{R_2 \times I_2}{I_2 - I_{RX}} \dots \dots \dots$$

After obtaining the I_{RX} , the I_2 can be obtained from two methods.

Method I

$$I_2 = I_3 - I_{RX} \dots \dots \dots$$

Method II

$$I_2 = \frac{(R_3 + R_X) I_3}{R_2 + R_3 + R_X} \dots \dots \dots$$

Instructions

- 1. For every value of R_X measure the I_2 value
- 2. Use the I_2 expression to estimate its value for all cases of R_X
- 3. Obtain the value of I_{RX} using both the millimeter, and the I_{RX} expression, and tabulate the results.

Current division principle

$$I_2 = \frac{V}{R_1 + [R_2 \parallel (R_3 + R_X)]} = \frac{9}{1 + [2 \parallel 1 + 0.1]} = \frac{9}{1 + 2 \parallel 1.1} = \frac{9}{1.71} = 5.26mA$$

$$I_2 = \frac{9}{1.73} = 5.20mA$$

$$I_2 = \frac{9}{1 + (2 \parallel 1.2)} = \frac{9}{1.75} = 5.14mA$$

$$i_{100} = \frac{9}{1 + (2 \parallel 1.4)} = \frac{9}{1.824} = 4.93mA$$

$$i_{100} = \frac{9}{1 + (2 \parallel 1.6)} = \frac{9}{1.888} = 4.76mA$$

$$i_{100} = \frac{9}{1 + (2 \parallel 1.8)} = \frac{9}{1.947} = 4.622mA$$

$$i_{100} = \frac{9}{1 + 2 \parallel 2} = \frac{9}{2} = 4.5mA$$

$$i_{100} = \frac{9}{1 + 2 \parallel 2.2} = \frac{9}{2.047} = 4.39mA$$

$$i_{100} = \frac{9}{1 + 2 \parallel 2.4} = \frac{9}{2.09} = 4.30mA$$


$$i_{100} = \frac{9}{1 + (2 \parallel 2.6)} = \frac{9}{2.13} = 4.22mA$$

$$= \frac{9}{1 + 2 \parallel 2.8} = \frac{9}{2.166} = 4.155mA$$

$$= \frac{9}{1 + 2 \parallel 3} = \frac{9}{2.2} = 4.09mA$$

Week 7

BRIGHTNESS CONTROL OF LEDS USING A POT

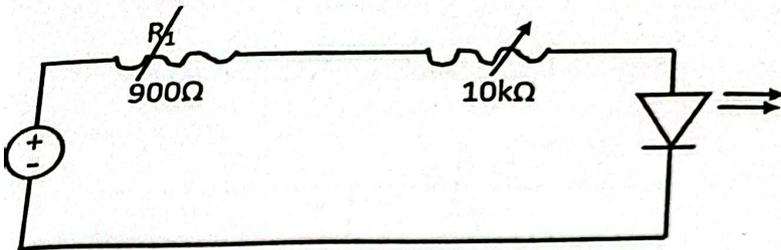


practical: the application of a potentiometer for controlling the brightness of an LED is demonstrated, the variable resistor is connected such that, as the PoT is turned clockwise, the LED gives more light. And if the PoT is turned in the counter-clockwise direction, the LED gives less light.

The function of the 900Ω fixed resistor is to ensure that the LED is protected from a short-circuit, when the PoT is turned counter clockwise to the end (zero resistance).

KIRCHHOFF'S VOLTAGE LAW (KVL)

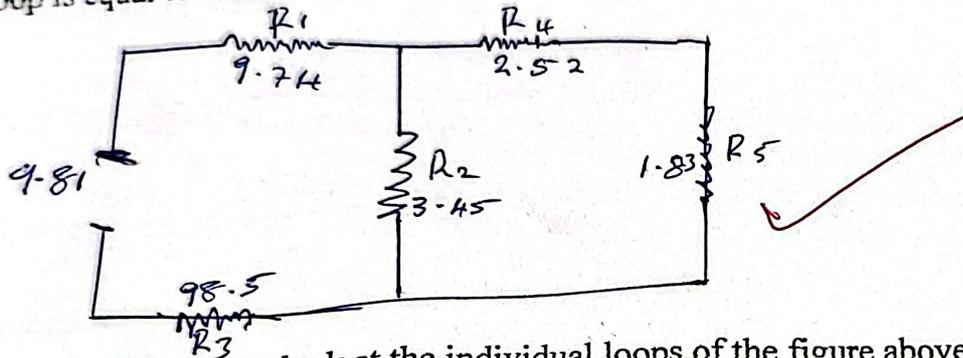Kirchhoff's voltage law (KVL) states that the algebraic sum of voltage in a closed loop is equal to zero.



To verify KVL, let us look at the individual loops of the figure above.

Loop 1, following the clockwise direction of the mesh current.

$$V_s + V_1 + V_2 + V_3 = 0$$

$$-V_2 + V_3 = V_s \dots \dots \dots (1)$$

2

second loop (loop 2), the voltage drop across R₂; i.e. V₂ serves as the voltage

Therefore, the expression is as follows;

$$V_4 + V_5 = 0$$

$$= V_2 \dots \dots \dots (2)$$

ation; The first loop voltages are as follows;

$$V_1 = \frac{R_1 V_s}{R_1 + R_2 + R_3} = \frac{1 \times 5}{1 + 2.4 + 1.2} \text{ V} = \frac{5}{4.6} = 1.086 \text{ V}$$

$$V_2 = \frac{R_2 V_s}{R_1 + R_2 + R_3} = \frac{2.4 \times 5}{4.6} \text{ V} = \frac{12}{4.6} = 2.60 \text{ V}$$

$$V_3 = \frac{R_3 V_s}{R_1 + R_2 + R_3} = \frac{1.2 \times 5}{4.6} \text{ V} = \frac{6}{4.6} = 1.304 \text{ V}$$

for the second loop, the voltages are as follows:

since $V_2 = 2.60 \text{ V}$ for loop 1,

$$V_4 = \frac{R_4 V_2}{R_4 + R_5} = \frac{1.2 \times 2.6}{1.2 + 1} = \frac{3.12}{2.2} \text{ V} = 1.418 \text{ V}$$

$$V_5 = \frac{R_5 V_2}{R_4 + R_5} = \frac{1 \times 2.6}{2.2} = 1.18 \text{ V}$$

procedure:

Connect the circuit as shown

Record the readings of the voltages in the table below:

| V_1 | V_2 | V_3 | V_4 | V_5 | V_s |
|-------|-------|-------|-------|-------|-------|
| 0.83 | 0.30 | 0.45 | 0.18 | 0.12 | 9.81 |

Using equation (1), and the figures in the table above, compute $V_1 + V_2 + V_3$

V_s

Using equation (2), compute $V_4 + V_5 = V_2$

[Handwritten signature]

Is KVL satisfied in the loop 1? If yes, how.....

2. Is the KVL satisfied in loop 2? If yes, how?